

Roll No.

Total No. of Pages : 02

Total No. of Questions : 16

**BCA (2014 to 2018 Batch) (Sem.-3)**  
**DIGITAL CIRCUITS AND LOGIC DESIGN**  
Subject Code : BSBC-303  
M.Code : 10059

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTIONS TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains SIX questions carrying TEN marks each and students have to attempt any FOUR questions.
3. Use of non-programmable scientific calculator is allowed.

**SECTION-A**

**Answer briefly :**

1. What is NAND gate?
2. What is half adder?
3. What is binary subtractor?
4. What is multiplexer?
5. Differentiate between RS and JK flip-flop.
6. Explain Synchronous counter.
7. What is race condition?
8. Covert octal 736.4 to decimal.
9. What is up-down counter?
10. What is 1's complement of 0001111?

## SECTION-B

11. Explain design of synchronous counters.
12. Explain different types of flip-flops.
13. Explain different types of logic gates.
14. Differentiate between :
  - a. encoder and decoder.
  - b. half adder and full adder
15. a. Explain MOD-N counters  
b. Convert the hexadecimal number F3A7C2 to binary and octal.
16. a. Simplify the Boolean function  $F(A,B,C,D) = \sum(3,7,11,13,14,15)$  in sum-of-products form.  
b. Explain the concept of binary adder.

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**