

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 07

B.Sc. (IT) (Sem-1)
COMPUTER SYSTEM ARCHITECTURE
Subject Code : UGCA-1908
M.Code : 76954
Date of Examination : 09-06-2023

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains SIX questions carrying TEN marks each and students have to attempt any FOUR questions.

SECTION-A

1. Write briefly :

- a) Explain in brief about NOR Gate. Write its truth table.
- b) Which Gates are called as the universal gates? Also write the advantages of Universal Gates.
- c) State the limitations of K-Maps.
- d) Define the term Binary Adder.
- e) What do you mean by a Decoder? Explain.
- f) Differentiate between Combinational & Sequential circuits?
- g) What is the operation of D flip-flop?
- h) What is the concept of Harvard architecture?
- i) What are Register reference Instructions. List any two Register reference instructions.
- j) What do you mean by Address Bus? Explain.

SECTION-B

2. a) **Explain about Boolean expression. Simplify the Boolean expression :**
$$F = C (B + C) (A + B + C).$$

b) Explain in detail about Realization of Boolean Expression using Gates.
3. Write a detailed note on SOP and POS Forms.
4. **Explain the following terms in detail :**
 - a) Half Subtractor.
 - b) Full Adder
5. **Explain the following terms in detail :**
 - a) Multiplexers
 - b) Encoders
6. **Explain the working of following flip-flops with a truth table and logic circuit :**
 - a) R-S Flip Flop
 - b) Master- Slave J-K Flip Flop
7. Explain the Von Neumann Architecture in detail.

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.